

MULTI-STAGE AMPLIFIERS

To analyze multistage amplifier the h-parameters of the transistor used are obtained from manufacture data sheet. The manufacture data sheet usually provides h-parameter in CE configuration. These parameters may be converted into CC and CB values. For example fig. 4 hrc in terms of CE parameter can be obtained as follows.

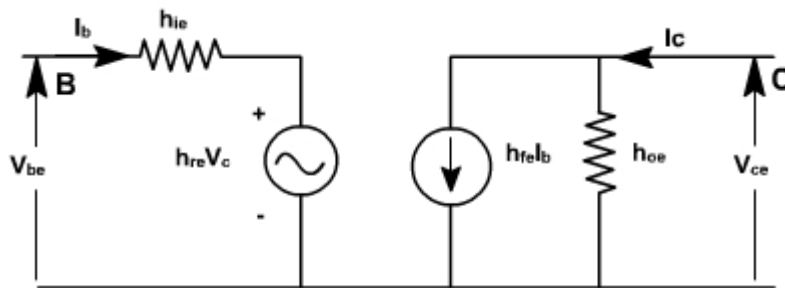


Fig. 4

For CE transistor configuration

$$V_{be} = h_{ie} I_b + h_{re} V_{ce}$$

$$I_c = h_{fe} I_b + h_{oe} V_{ce}$$

The circuit can be redrawn like CC transistor configuration as shown in fig. 5.

$$V_{bc} = h_{ie} I_b + h_{rc} V_{ec}$$

$$I_c = h_{fe} I_b + h_{oe} V_{ec}$$

$$\begin{aligned}
 h_{rc} &= \left. \frac{V_{be}}{V_{ec}} \right|_{I_b=0} \\
 &= \left. \frac{V_{be} + V_{ec}}{V_{ec}} \right|_{I_b=0} \\
 &= \left. \left(\frac{V_{be}}{V_{ec}} + 1 \right) \right|_{I_b=0}
 \end{aligned}$$

Since $I_b = 0$, $V_{be} = h_{re} V_{ce} = -h_{re} V_{ec}$

$$\begin{aligned}
 \therefore h_{rc} &= 1 + \left(\frac{h_{re} V_{ec}}{V_{ec}} \right) \\
 &= 1 - h_{re}
 \end{aligned}$$

Similarly

$$\begin{aligned}
 h_{fc} &= \left. \frac{I_e}{I_b} \right|_{V_{ec}=0} = \left. \frac{-(I_b + I_c)}{I_b} \right|_{V_{ec}=0} \\
 &= -(1 + h_{fe})
 \end{aligned}$$

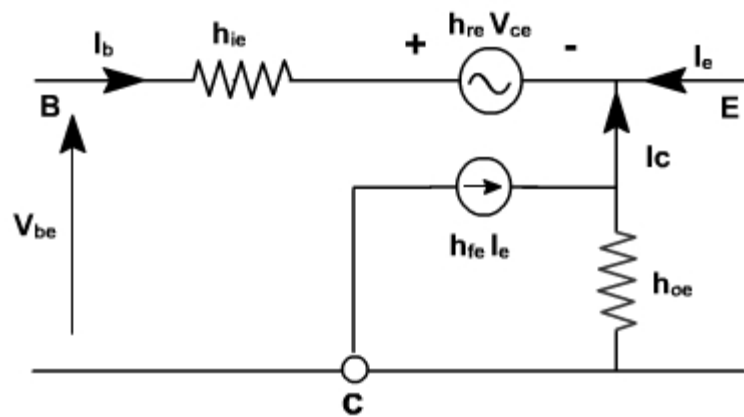


Fig. 5