

FILTERS

The output of rectifier is pulsating DC (DC component + ac component). The filters are used to convert pulsating DC to pure DC. The full wave rectifier gives ac component of 0.482 times the dc component. Where as HWR has ac component = 1.21 times the dc component. Therefore it is better to connect output of FWR to filter circuit.

Ideally the output of filter is pure DC (the AC component should be zero). But practically the filter circuit will minimize the ripples at output as far as possible. (amount of AC ripple is less and negligible in comparison with AC ripple at output of rectifier).


There are different types of filters:

1. Inductor filter
2. Capacitor filter
3. LC or L-Section filter
4. CLC or π -section filter
5. Multiple L-Section filter
6. Multiple π -section filter

Harmonic components in the rectifier circuits :

A mathematical representation of output current waveform in rectifier is obtained by means of Fourier series.

FOR HWR:

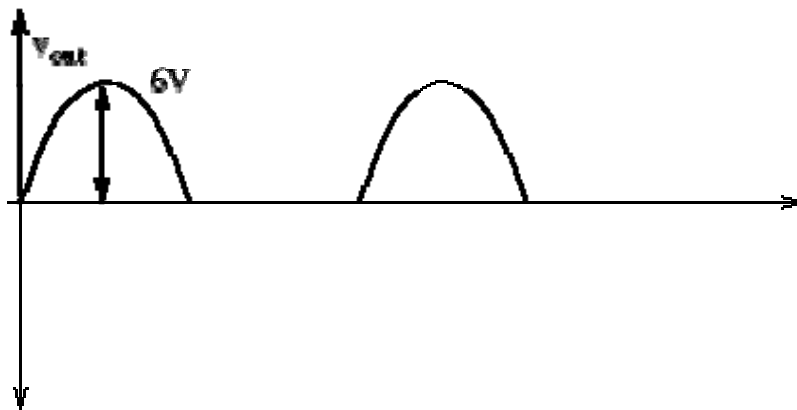

$$i = I_m \left[\frac{1}{\pi} + \frac{1}{2} \sin \omega t - \frac{2}{\pi} \sum_{k=2,4,6,\dots} \frac{\cos k\omega t}{(k+1)(k-1)} \right]$$

The DC component Here is $\frac{I_m}{\pi}$

The lowest angular frequency present in active equation is that of primary source of AC power (fundamental frequency).

All other terms in above expression are even harmonics of power frequency.

For FWR

$$i = I_m \left[\frac{2}{\pi} - \frac{4}{\pi} \sum_{k=2,4,6,\dots} \frac{\cos k\omega t}{(k+1)(k-1)} \right]$$

Problems:

1. A 230V, 60Hz voltage is applied to 5:1 step down centre tapped transformer used in FWR circuit having a load of 900Ω . If diode resistance and secondary coil resistance together has 100Ω . Calculate
 - i. dc voltage across load.
 - ii. dc current flowing load
 - iii. dc power delivered to load
 - iv. PIV across each diode
 - v. ripple voltage

sol. $\frac{e_1}{e_2} = \frac{N_1}{N_2}$

$$\frac{230}{e_2} = \frac{5}{1} \Rightarrow e_2 = 46V$$

Secondary voltage of transformer = 46V

Voltage from centre tapping to each end = 23V

Load resistance, $R_L = 900\Omega$

$$R_f + R_s = 100\Omega$$

Total resistance = $1k\Omega$

$$\begin{aligned} \text{i. } V_m &= V_{rms} \cdot \sqrt{2} \\ &= 23\sqrt{2} = 32.52 \end{aligned} \quad V_{dc} = \frac{2V_m}{\pi} = 20.7$$

$$\begin{aligned} \text{ii. } I_{dc} &= \frac{V_{dc}}{R} = \frac{20.7}{10^3} \\ &= 20.7mA \end{aligned}$$

$$\begin{aligned} \text{iii. } P_{dc} &= I_{dc} \cdot V_{dc} \\ &= (20.7)(20.7 \times 10^{-3}) \\ &= 428.64 \times 10^{-3} = 0.428W \end{aligned}$$

$$\begin{aligned} \text{iv. } PIV &= 2V_m \\ &= 2(32.52)V = 65.04V \end{aligned}$$

$$\begin{aligned} \text{v. } \text{Ripple voltage} &= V_{ac} = \\ &= V'_{rms} \\ &= \sqrt{V_{rms}^2 - V_{dc}^2} \\ &= \sqrt{(23)^2 - \left(\frac{2(23\sqrt{2})}{\pi}\right)^2} \\ &= \sqrt{(23)^2 - (20.7)^2} \\ &= 10.02V \end{aligned}$$

Since here ripple voltage means rms value of ac component in output of rectifier.