

## PROBLEMS

Select  $R_1$  and  $R_2$  for maximum output voltage swing in the circuit shown in fig. 5.

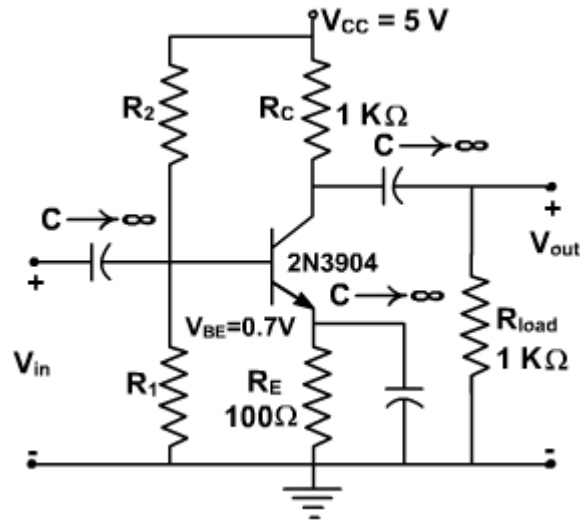


Fig. 5

Solution:

We first determine  $I_{CQ}$  for the circuit

$$R_{ac} = R_C \parallel R_{load} = 500$$

$$R_{dc} = R_E + R_C = 1100$$

$$I_{CQ} = \frac{V_{CC}}{R_{ac} + R_{dc}} = \frac{5}{500 + 1100} = 3.13 \text{ mA}$$

For maximum swing,

$$V'_{CC} = 2 V_{CEQ}$$

The quiescent value for  $V_{CE}$  is the given by

$$V_{CEQ} = (3.13 \text{ mA}) (500 \Omega) = 1.56 \text{ V}$$

K.CHIRANJEEVI,ECE,GMRIT

The intersection of the ac load line on the  $v_{CE}$  axis is  $V'_{CC} = 3.13V$ . From the manufacturer's specification,  $\beta$  for the 2N3904 is 180.  $R_B$  is set equal to  $0.1 \beta R_E$ . So,

$$R_B = 0.1(180)(100) = 1.8 \text{ K } \Omega$$

$$V_{BB} = (3.13 \times 10^{-3})(1.1 \times 100) + 0.7 = 1.044 \text{ V}$$

Since we know  $V_{BB}$  and  $R_B$ , we find  $R_1$  and  $R_2$ ,

$$R_1 = \frac{R_B}{1 - V_{BB}/V_{CC}} = \frac{1800}{1 - 1.044/5} = 2.28 \text{ K}\Omega$$

$$R_2 = \frac{R_B V_{CC}}{V_{BB}} = \frac{1800 \times 5}{1.044} = 8.62 \text{ K}\Omega$$

The maximum output voltage swing, ignoring the non-linearity's at saturation and cutoff, would then be

$$\begin{aligned} \text{Max collector current swing} &= 2 I_{CQ} (R_C \parallel R_{load}) \\ &= 2 (3.13 \text{ mA}) (500 \Omega) = 3.13 \text{ V} \end{aligned}$$

The load lines are shown on the characteristics of fig. 6.

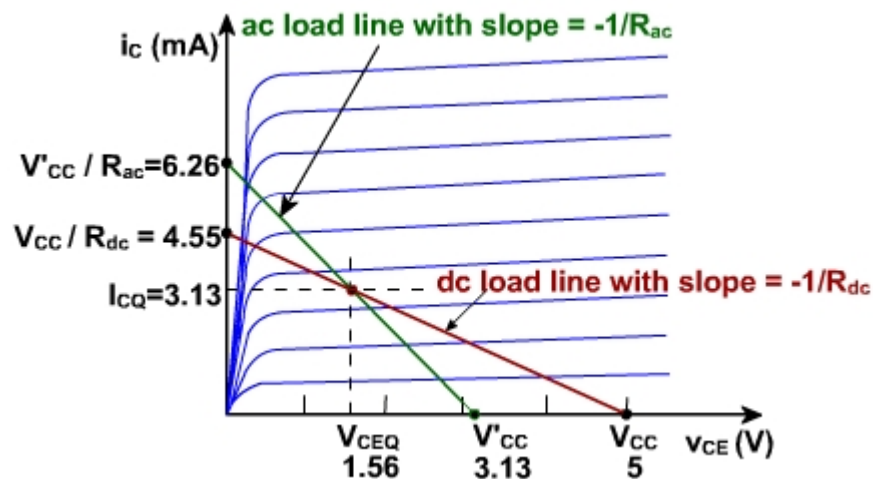


Fig. 6

The maximum power dissipated by the transistor is calculated to assure that it does not exceed the specifications. The maximum average power dissipated in the transistor is

$$P_{(\text{transistor})} = V_{CEQ} I_{CQ} = (1.56 \text{ (V)}) (3.13 \text{ mA}) = 4.87 \text{ mW}$$

This is well within the 350 mW maximum given on the specification sheet. The maximum conversion efficiency is

$$\eta = \frac{P_{\text{out(ac)}}}{P_{V_{CC}(\text{dc})}} = \frac{(3.13 \times 10^{-3} / 2)^2 \times 1000 / 2 \times 100}{5 \times 3.13 \times 10^{-3} + 5^2 / 10.9 \times 10^3} = 6.84\%$$

The swamped Amplifier:

The ac resistance of the emitter diode  $r'_e$  equals  $25\text{mV} / I_E$  and depends on the temperature. Any change in  $r'_e$  will change the voltage gain in CE amplifier. In some applications, a change in voltage is acceptable. But in many applications we need a stable voltage gain is required.

To make it stable, a resistance  $r_E$  is inserted in series with the emitter and therefore emitter is no longer ac grounded. fig .7.

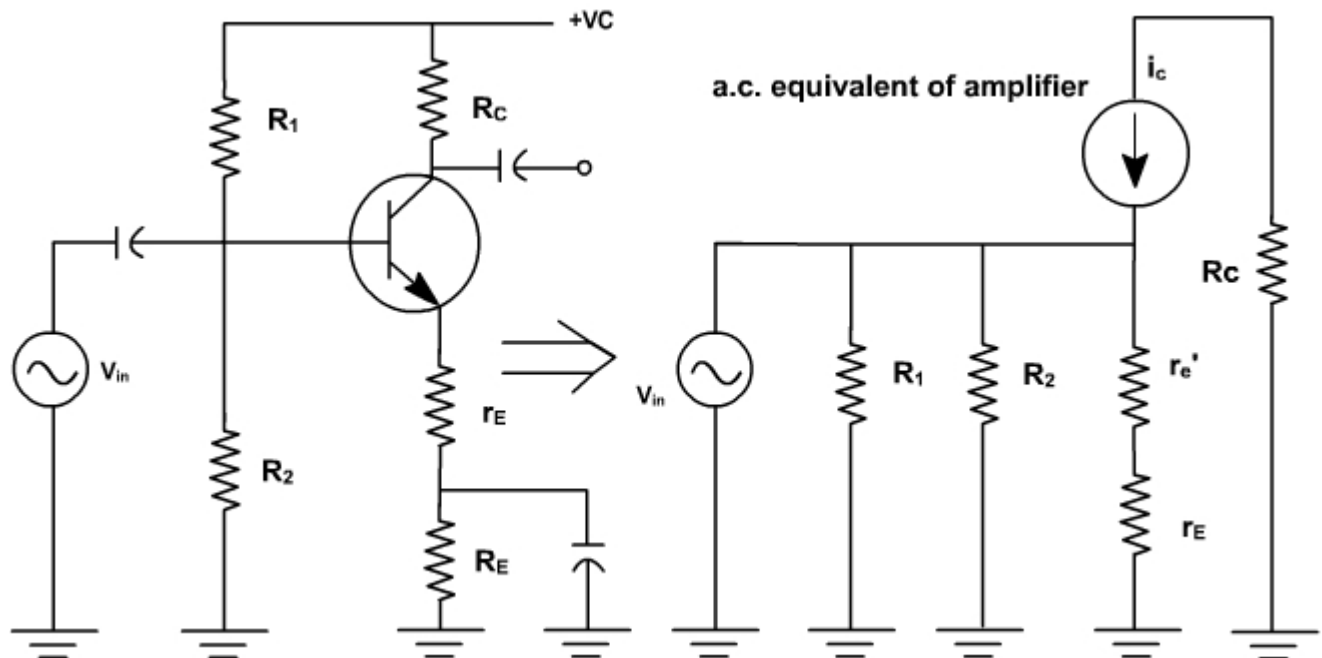


Fig. 7

Because of this the ac emitter current flows through  $r_E$  and produces an ac voltage at the emitter. If  $r_E$  is much greater than  $r'_e$  almost all of the ac input signal appears at the emitter, and the emitter is bootstrapped to the base for ac as well as for dc.

In this case, the collector circuit is given by

$$i_C = \frac{V_{in}}{r'_e + r_E}$$

and  $V_{out} = -i_C R_C$

Therefore,

$$A = \frac{V_{out}}{V_{in}} = -\frac{i_C R_C}{i_C (r'_e + r_E)}$$

$$= -\frac{R_C}{(r'_e + r_E)}$$

Now  $r'_e$  has a less effect on voltage gain, swamping means  $r_E \gg r'_e$ . If swamping is less, voltage gain varies with temperature. If swamping is heavy, then gain reduces very much.

Design a common-emitter amplifier with a transistor having a  $\beta = 200$  and  $V_{BE} = 0.7$  V. Obtain an overall gain of  $|A_V| \geq 100$  and maximum output voltage swing. Use the CE configuration shown in fig. 1 with two power supplies.  $R_{source}$  is the resistance associated with the source,  $V_{source}$ . Let  $R_{source} = 100$  Ohms. The output load is  $2K\Omega$ . Determine the resistor values of the bias circuitry, the maximum undistorted output voltage swing, and the stage voltage gain.

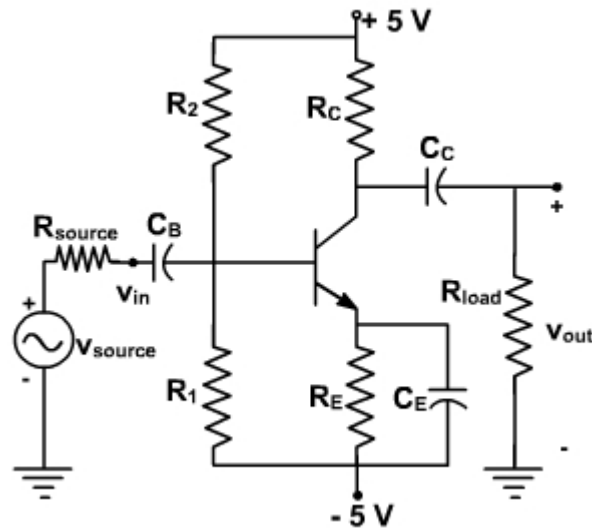


Fig. 1

Solution:

The maximum voltage across the amplifier is 10 V since the power supply can be visualized as a 10V power supply with a ground in the center. In this case, the ground has no significance to the operation of the amplifier since the input and output are isolated from the power supplies by capacitors.

We will have to select the value for  $R_C$  and we are really not given enough information to do so. Let choose  $R_C = R_{load}$ .

We don't have enough information to solve for  $R_B$  – we can't use the bias stability criterion since we don't have the value of  $R_E$  either. We will have to (arbitrarily) select a value of  $R_B$  or  $R_E$ . If this leads to a contradiction, or “bad” component values (e.g., unobtainable resistor values), we can come back and modify our choice. Let us select a value for  $R_E$  that is large enough to obtain a reasonable value of  $V_{BB}$ . Selecting  $R_E$  as  $400\Omega$  will not appreciably reduce the collector current yet it will help in maintaining a reasonable value of  $V_{BB}$ . Thus,

$$R_B = 0.1 \beta R_E = 0.1 (200)(400) = 8 \text{ K } \Omega$$

To insure that we have the maximum voltage swing at the output, we will use

$$I_{CQ} = \frac{V_{CC}}{R_{ac} + R_{dc}} = \frac{10}{1000 + 2400} = 2.94 \text{ mA}$$

$$V_{BB} = V_{BE} + I_{CQ} (R_B / \beta + R_E) = 0.7 + 2.9 \times 10^{-3} \left( \frac{8000}{200} + 400 \right) = 1.99 \text{ V}$$

Note that we are carrying out our calculations to four places so that we can get accuracy to three places. The bias resistors are determined by

$$R_1 = \frac{R_B}{1 - V_{BB}/V_{CC}} = \frac{8000}{1 - 1.99/10} = 9.99 \text{ K}\Omega$$

$$R_2 = R_B \frac{V_{CC}}{V_{BB}} = 8000 \left( \frac{10}{1.99} \right) = 40.2 \text{ K}\Omega$$

Since we designed the bias circuit to place the quiescent point in the middle of the ac load line, we can use

$$V_{out}(\text{undistorted p-p}) = 1.8 (2.94 \times 10^{-3}) (2 \text{ K}\Omega \parallel 2 \text{ K}\Omega) = 5.29 \text{ V}$$

Now we can determine the gain of the amplifier itself.

$$|A_v| = g_m (R_C \parallel R_{load}) = \frac{2.94 \times 10^{-3} \times 1000}{26 \times 10^{-3}}$$

Using voltage division, we can determine the gain of the overall circuit.

The value of  $R_{in}$  can be obtained as

$$R_{in} = r_{\pi} \parallel R_B = 1.77 \text{ k}\Omega \parallel 8 \text{ k}\Omega = 1.45 \text{ k}\Omega$$

Thus the overall gain of the amplifier is

$$|A_v|_{\text{overall}} = \left| \frac{v_{out}}{v_{in}} = 113 \right| \times \frac{R_{in}}{R_{in} + R_{source}} = 106$$

This shows that the common-emitter amplifier provides high voltage gain. However, it is very noisy, it has a low input impedance, and it does not have the stability of the emitter resistor common emitter amplifier.