

TRANSISTOR BISINGN

Find the transistor current in the circuit shown in **fig. 5**, if $I_{CO} = 20\text{nA}$, $\beta = 100$.

Solution:

For the base circuit, $5 = 200 \times I_B + 0.7$

Therefore,
$$I_B = \frac{5 - 0.7}{200k} = 0.0215\text{mA}$$

Since $I_{CO} \ll I_B$, therefore, $I_C = \beta I_B = 2.15\text{ mA}$

From the collector circuit, $V_{CE} = 10 - 3 \times 2.15 = 3.55\text{ V}$

Since, $V_{CE} = V_{CB} + V_{BE}$

Thus, $V_{CB} = 3.55 - 0.7 = 2.55\text{ V}$

Therefore, collector junction is reverse biased and transistor is operating in its active region.

Example - 2

If a resistor of 2K is connected in series with emitter in the circuit as shown in **fig. 6**, find the currents. Given $I_{CO} = 20\text{ nA}$, $\beta = 100$.

Solution:

$$I_E = I_B + I_C = I_B + 100 I_B = 101 I_B$$

For the base circuit, $5 = 200 \times I_B + 0.7 + 2k \times 101 I_B$

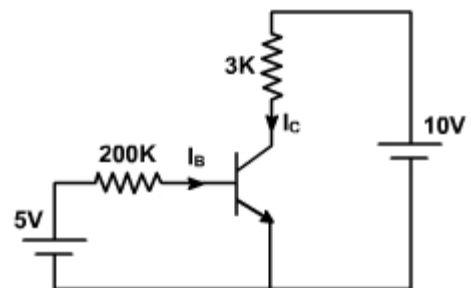


Fig. 5

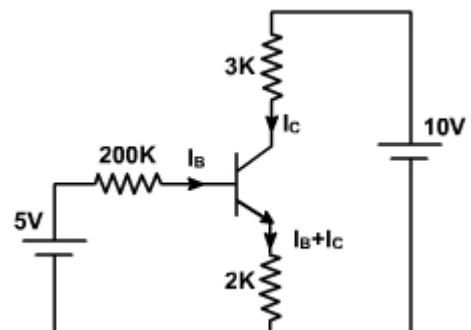


Fig. 6

Therefore,
$$I_B = \frac{5 - 0.7}{402k} = 0.0107 \text{ mA}$$

Since $I_{CO} \ll I_B$, therefore, $I_C = \beta I_B = 1.07 \text{ mA}$

From the collector circuit,
$$V_{CB} = 10 - 3 \times 1.07 - 0.7 - 2 \times 101 \times 0.0107 = 3.93 \text{ V}$$

Therefore collector junction is reverse biased and transistor is operating in its active region.

Example - 3

Repeat the **example-1** if R_B is replaced by 50k.

Solution:

The circuit is shown in **fig. 7**.

Since the base resistance is reduced, the base current must have increased and there is a possibility that the transistor has entered into saturation region.

Assuming transistor is operating in its saturation region,

$$V_{BE(sat)} = 0.8 \text{ V and } V_{CE(sat)} = 0.2 \text{ V}$$

Therefore,
$$I_B = \frac{5 - 0.8}{50k} = 0.0840 \text{ mA}$$

and
$$I_C = \frac{10 - 0.2}{3k} = 3.267 \text{ mA}$$

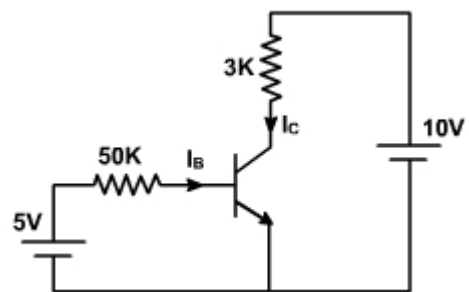


Fig. 7

The minimum base current required for operating the

transistor in saturation region is

$$I_{B(\min)} = \frac{I_C}{\beta} = 0.03267 \text{ mA}$$

Since $I_B > I_{B(\min)}$, therefore, transistor is operating in its saturation region.

Example - 4

Repeat the **example-2** if R_B is replaced by 50k.

Solution:

The circuit is shown in **fig. 8**.

Since the base resistance is reduced, the base current must have increased and there is a possibility that the transistor has entered into saturation region.

Assuming transistor is operating in its saturation region,

$$5 = 50 I_B + 0.8 + 2 \times (I_B + I_C)$$

$$10 = 3 I_C + 0.2 + 2 \times (I_B + I_C)$$

Solving these equations, we get,

$$I_C = 1.96 \text{ mA and } I_B = 0.0035 \text{ mA}$$

The minimum base current required for operating the transistor in saturation region is

$$I_{B(\min)} = \frac{I_C}{\beta} = 0.0196 \text{ mA}$$

K.CHIRANJEEVI,ECE,GMRIT

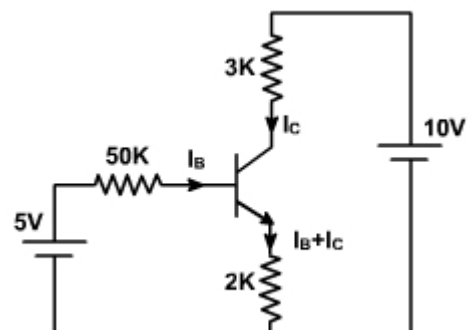


Fig. 8

Since $I_B < I_{B(\min)}$, therefore, transistor is operating in its **active** region and not in saturation. The base and the collector currents can be recalculated assuming the transistor to be in active region.

For the base circuit, $5 = 50 \times I_B + 0.7 + 2k \times 101 I_B$

Therefore,
$$I_B = \frac{5 - 0.7}{252k} = 0.0171 \text{ mA}$$

$$I_C = 1.71 \text{ mA}$$

From the collector circuit, $V_{CB} = 10 - 3 \times 1.71 - 0.7 - 2 \times 101 \times 0.0171 = 0.716 \text{ V}$